

Limitations of [[Finite State Machines]]


- previous state machines designed for specific application
- application changes require new state machine, new hardware
- general-purpose machine wanted

Von Neumann Model

- architecture with following components

- Processing Unit
- Control Unit
- Memory
- Input
- Output
- Buses

 -
- CPU connected via bus system to memory and I/O




-
- Harvard Architecture Variation
 - Memory split into Data and Instruction Memory

Arithmetic Logic Unit

- ALUs are [[Combinational Circuits]] performing calculation operations
- basic properties
 - Takes two n-bit inputs (A, B); today typically 32 bit or 64 bit
 - Performs an operation based on one or both inputs; the performed operation is selected by the control input `alu_sel`
 - Returns an n-bit output; It typically also provides a status output with flags to e.g. indicate overflows or relations of A and B, such as $A==B$ or $A<B$

Register File

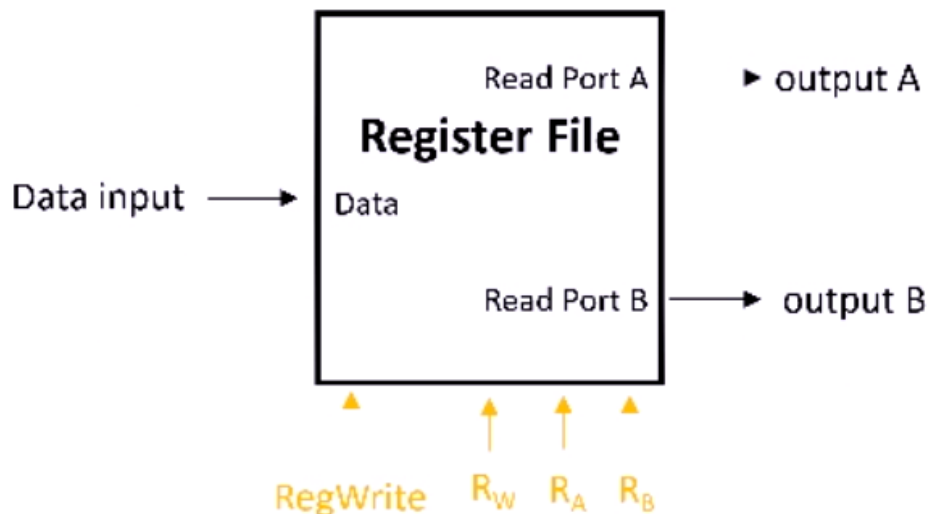
- contains m n-bit registers
- write one n-bit value per clock cycle
 - register selected via R_W
 - does not write if low
- read two registers per clock cycle
 - provided at outputs A and B
 - registers selected via R_A and R_B
- basically memory with
 - one write port
 - two read ports



-
- register file with 32 registers


- **Basic Properties**

 - Data registers with two output MUX
- Input is stored in any one of the registers (selection via R_W signal)
- Typical register sizes: 8, 16, 32, 64 bit



Processing Unit

- combines ALU and register file

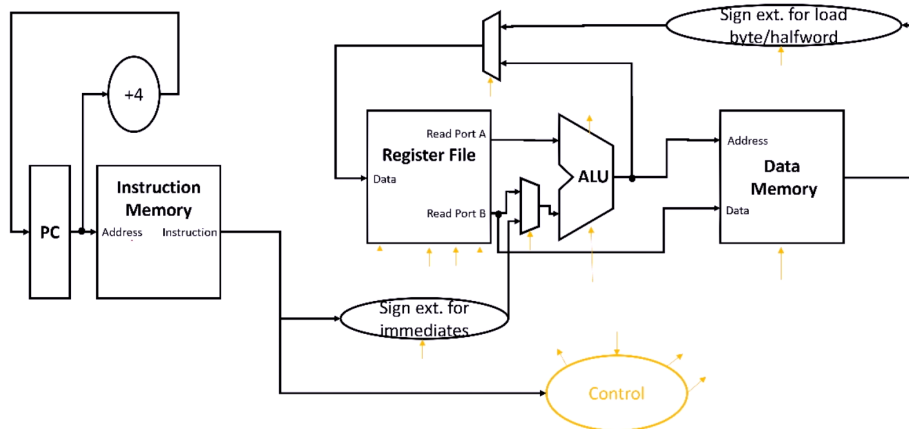

- instruction register
 - stores instruction to execute and parameters
 - mapped to control signals by instruction encoder

