

Types of [[Finite State Machines]]


Moore Machines

- next state = function of present state and input
- output = function of present state


Mealy Machines

- next state = function of present state and input
- output = function of present state **and input**
- mealy machines have different outputs for the same state
 - output written outside of state circle
 - next to state transition
 - value of input affect timing diagram


state	in	output
A	0	4
A	1	4
B	0	3
B	1	1
C	0	2
C	1	0

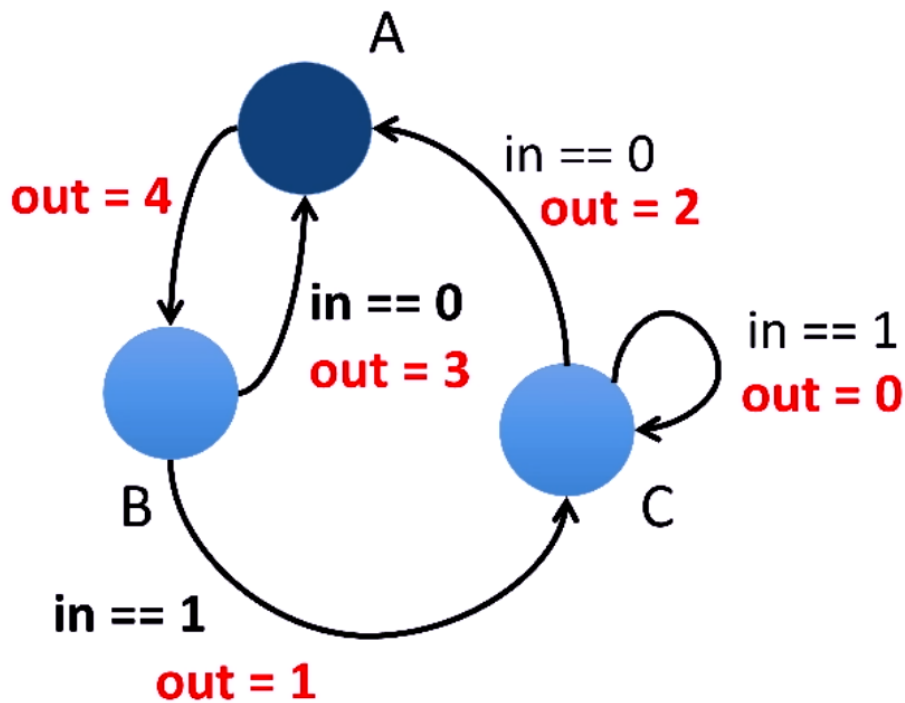

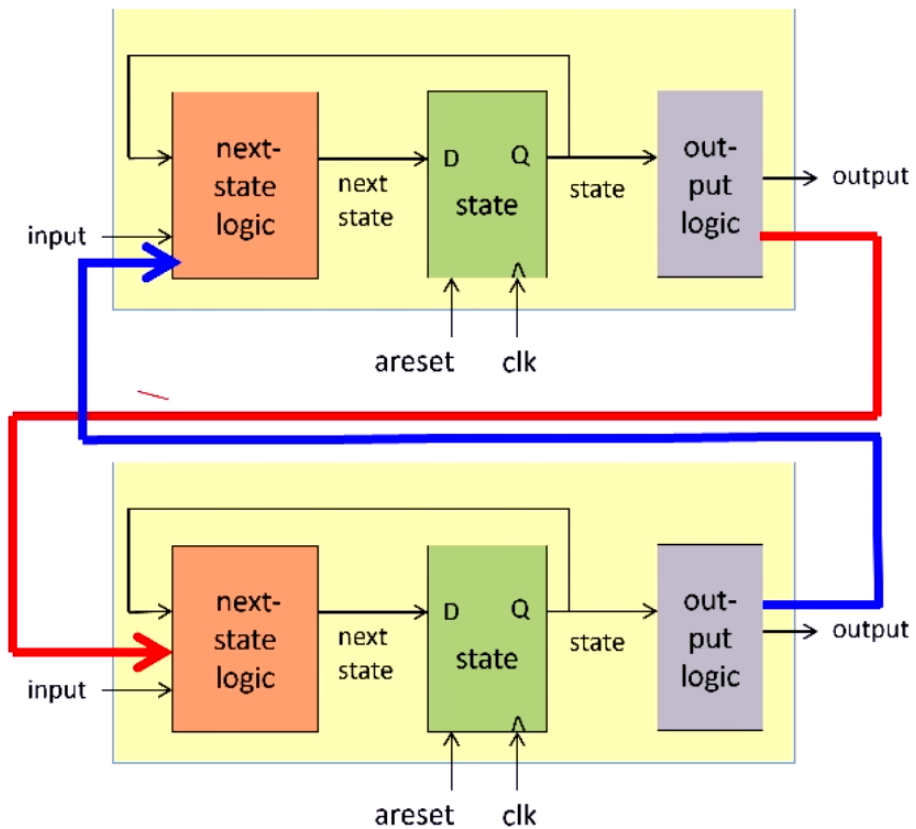- machine combinations
 - multiple moore machines cause no problems



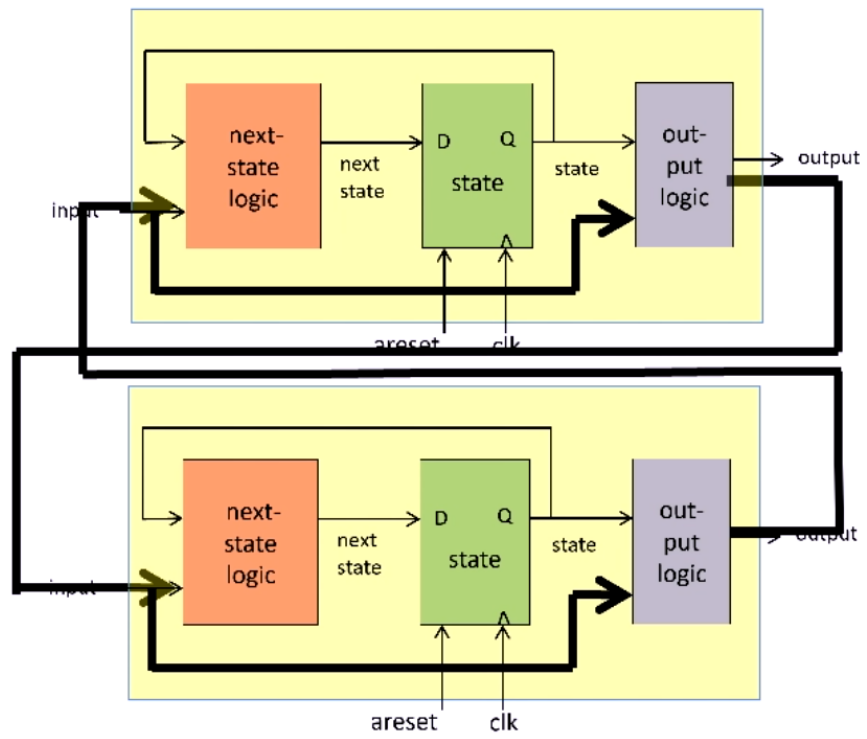- *
 - moore with mealy machine cause no problems
 - two mealy machine may cause problems
 - * one needs to avoid combinational loops



*