

Overview

- PMOS
 - conducting if A connected to GND



—

- NMOS
 - conducting if connected to Vdd



—

- similar to switches
 - PMOS: $A=0 \rightarrow$ switch is open; $A=1 \rightarrow$ switch is closed
 - NMOS: $A=0 \rightarrow$ switch is closed; $A=1 \rightarrow$ switch open
- combine multiple transistors for computational logic and storage
 - [[Logic Gates]]