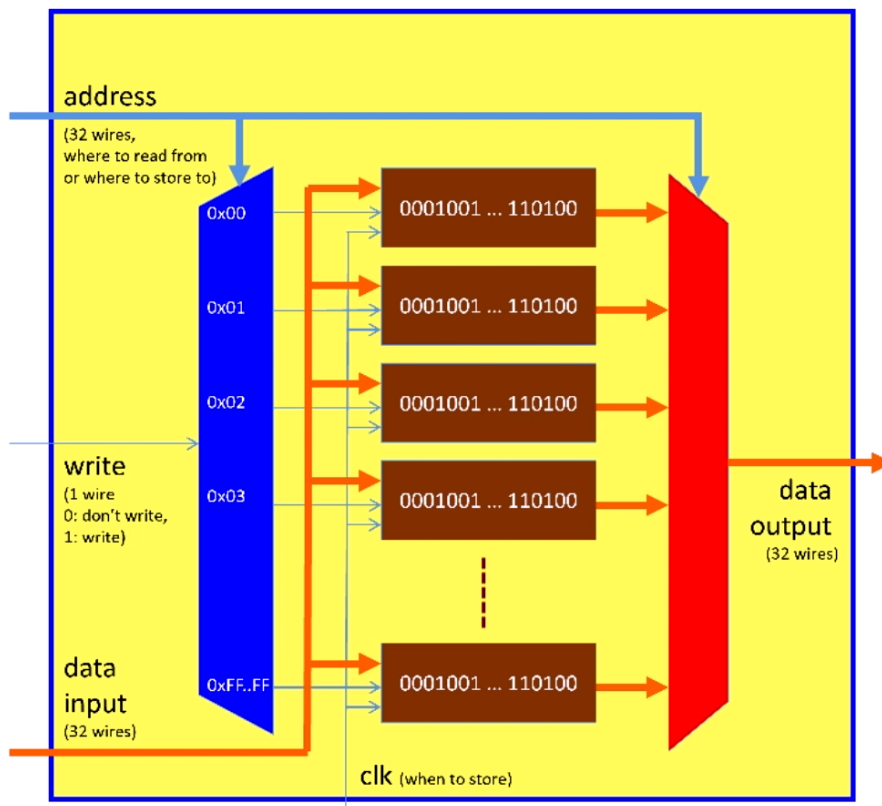



Memory

- Random Access Memory
 - store data at arbitrary (random) location in memory



Endiannes

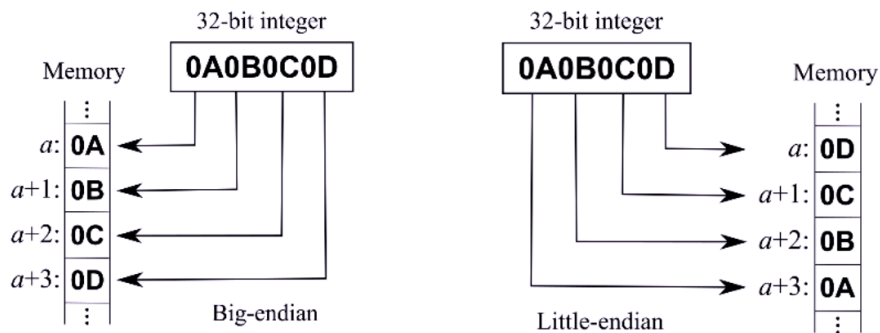- little endian
 - LSB at lowest address
- big endian
 - MSB at lowest address



Building Memory

- standard flip flops, decoders and multiplexer would be expensive

- able to write/read value to each FF in each cycle
- not necessary for most memory
- single port to read/write memory
 - read/write one cell at a time

Basic Idea of Memory Design

- A bitline connects all memory cells of a column vertically (yellow)
 - A wordline connects all memory cells of a row horizontally
 - This basic structure is used for all kinds of memories:
 - Non-volatile memory (NVM)
 - Static memory (SRAM)
 - Dynamic memory (DRAM)
 - DDR memory
 - Each memory type is for different trade-offs with respect to size, speed, ...
 - DRAM
 - A DRAM cell just consists of a single transistor and a capacitance that stores the data value
 - In steady state (no access) all bitlines and wordlines are disconnected from the power supply (i.e. they are floating)
-
- Writing a cell:
- Set corresponding bitline to the desired storage value
 - Set corresponding wordline to high
 - This charges the capacitance of the desired cell to the desired storage value
- Reading a cell:
- Pre-charge the corresponding bitline to the desired voltage value
 - Disconnect the bitline
 - Set the corresponding wordline to high
 - The bitline keeps its value, if the stored value is high or is pulled to low, if the stored value is zero
-

