

## Limitations of [[Finite State Machines]]


- previous state machines designed for specific application
- application changes require new state machine, new hardware
- general-purpose machine wanted

## Von Neumann Model

- architecture with following components

- Processing Unit
- Control Unit
- Memory
- Input
- Output
- Buses

 - CPU connected via bus system to memory and I/O



- Harvard Architecture Variation
  - Memory split into Data and Instruction Memory

## Arithmetic Logic Unit

- ALUs are [[Combinational Circuits]] performing calculation operations
- basic properties

Takes two n-bit inputs (A, B); today typically 32 bit or 64 bit


Performs an operation based on one or both inputs; the performed operation is selected by the control input `alu_sel`

Returns an n-bit output; It typically also provides a status output with flags to e.g. indicate overflows or relations of A and B, such as  $A=B$  or  $A<B$

—
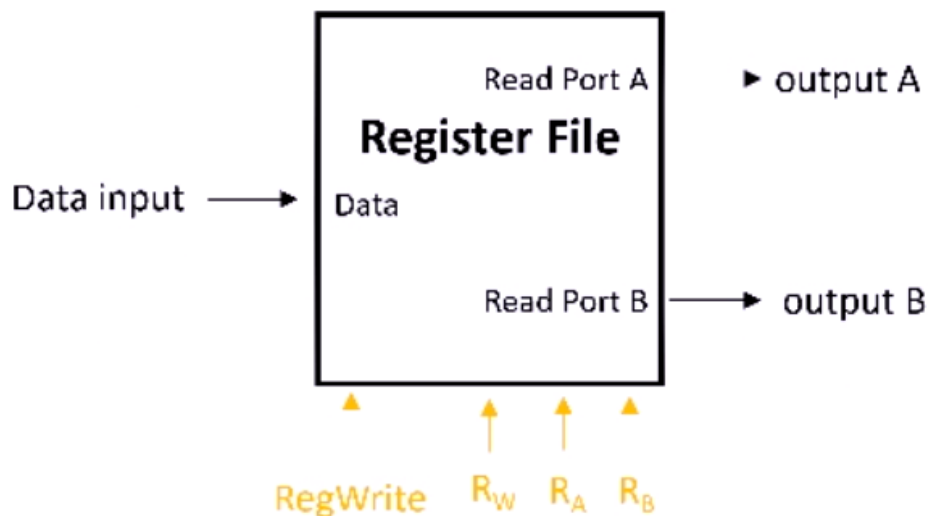
## Register File


- contains m n-bit registers
- write one n-bit value per clock cycle
  - register selected via  $R_W$
  - does not write if low
- read two registers per clock cycle
  - provided at outputs A and B
  - registers selected via  $R_A$  and  $R_B$
- basically memory with
  - one write port
  - two read ports



- 
- register file with 32 registers


- **Basic Properties**

 - Data registers with two output MUX
- Input is stored in any one of the registers (selection via  $R_W$  signal)
- Typical register sizes: 8, 16, 32, 64 bit



## Processing Unit

- combines ALU and register file

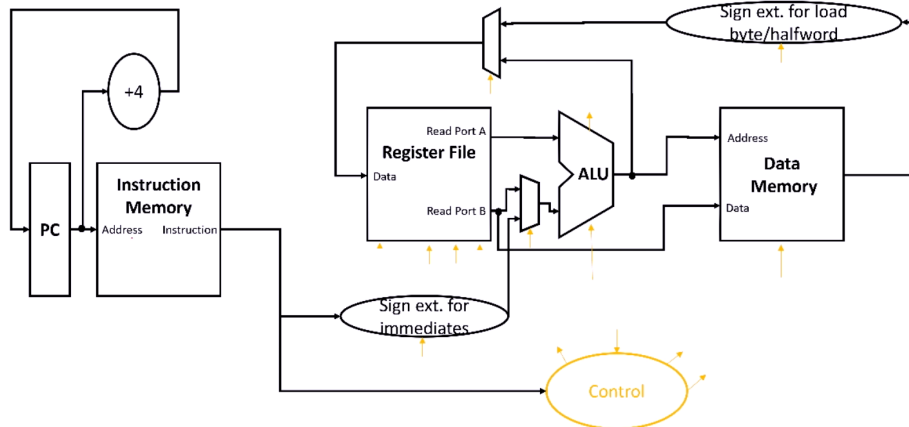

- instruction register
  - stores instruction to execute and parameters
  - mapped to control signals by instruction encoder

